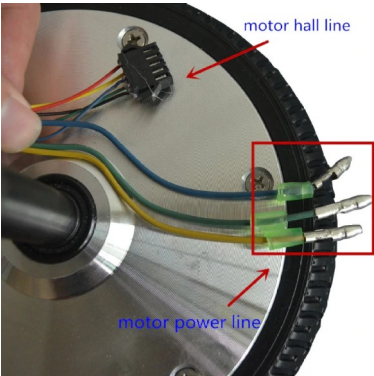


Motor (phase) lines:  
\*Green  
\*Blue  
\*Yellow




Motor (phase) lines:  
\*Green  
\*Blue  
\*Yellow

Electric motor whell  
from howerboard




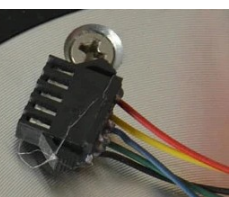Hall:  
\*Black: ground wire  
\*blue: hall  
\*Green: hall  
\*Yellow: hall  
\*red 5 v positive



Hall:  
\*Black: ground wire  
\*blue: hall  
\*Green: hall  
\*Yellow: hall  
\*red 5 v positive

Handle 3 wire switch  
(throttle):

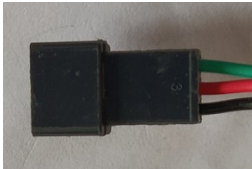

Throttle (lever)  
\*Green: throttle hall signal,  
\*Red: throttle +5v  
\*Black: negative wire

“please connect according to controller  
function wire, U can not just match  
same color wire, if wrong connected  
that will damage your controller and  
throttle. “

throttle/switch/lcd



Red: 5 volts positive  
Green: signal wire  
Black: ground wire



Power wires:

\*thick red: positive power  
supply battery

\*thick black: negative  
power supply battery


\*thin red: electric door lock  
switch

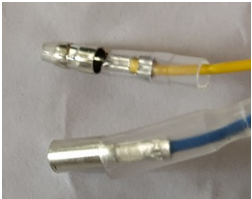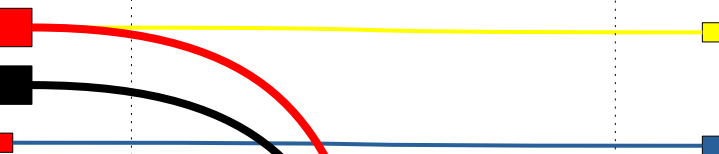(if you don't use switch,  
connect thin red, and thick  
red wire directly)



On off switch (on the throttle):  
\*Yellow wire: controller electric  
switch input wire power positive  
(positive power supply battery)

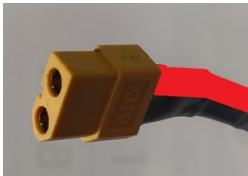
\*Blue wire: controller power lock  
output wire (electric door lock  
switch)



Self study:  
if the wheel is rotating in the  
wrong direction:  
Turn off using switch,  
connect two wires together  
Turn on, check direction.  
If ok, turn off, disconnect,  
and power on again (?)

Low voltage brake wire:

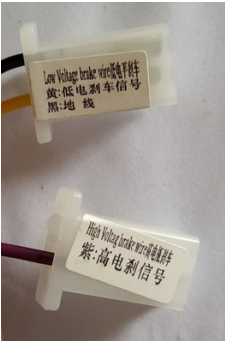\*black ground wire  
\*yellow low electric brake  
signal



High Voltage brake wire  
\*Purple: high electric brake  
signal

(Brake does not seem to  
work? Just cuts power off,  
like off switch)



Speed meter  
(connect to speed  
meter lcd if you  
have one, optional)



Battery:  
\*red (square end): +  
\*black (round end): -

Battery 36v 4.4Ah (or more Ah)  
(18650x20 + bms, 10s2p probably)

